

Paper Code : 21306**F-406****B. C. A. (Second Semester)
EXAMINATION, 2019
(New Course)**

Paper No. BCA— (N)—201

DIGITAL ELECTRONICS**Time : Three Hours]****[Maximum Marks : 70****Note : Attempt any five questions. All questions carry equal marks.****1. (a) Perform the following conversions :**

(i) $(ABC)_{16} = (?)_{10}$

(ii) $(47.6)_8 = (?)_{10}$

(iii) $(5137)_{10} = (?)_{BCD}$

(iv) $(62.7)_8 = (?)_{16}$

(b) Find 9's and 10's complements of the following decimal numbers :

(i) 2431

(ii) 5299

(B-6) P. T. O.**2. (a) What do you mean by the base of a number system ? Give examples to illustrate the role of base in positional number system.****(b) What is logic gates ? Discuss the various types of gates. Why is the NAND gate called Universal gate ?****3. (a) Simplify the following Boolean function, using Karnaugh maps :**

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 10, 13)$$

(b) Express the Boolean function :

$$F = AB + AC + AD$$

in sum of minterms form.**4. (a) State and prove two basic De-Morgan's theorems.****(b) Convert the given expression in standard POS form : <http://www.mjpruonline.com>**

$$f(A, B, C) = (A + B)(B + C)(A + C)$$

(c) What do you mean by general switching problem ?**5. (a) Implement a full adder and explain.****(b) Design a full adder using NAND gates.****6. Differentiate between the following :****(i) Multiplexer and De-multiplexer****(ii) Combinational and Sequential circuit****(iii) POS and SOP****(iv) Analog and Digital signal****(v) Serial and Parallel register**

7. (a) Explain the working of master slave JK flip-flop.
(b) What is race around condition ? Explain in brief.
(c) How can one convert D flip-flop to T flip-flop ? Explain.
8. Write short notes on the following (any four) :
 - (i) Floating point number representation
 - (ii) Counters
 - (iii) Venn diagram representation of Boolean algebra
 - (iv) Signed and unsigned number representation
 - (v) Encoders
 - (vi) Weighted number systems